



ASSESSMENT and
QUALIFICATIONS
ALLIANCE

Mark scheme January 2003

GCE

Physics A

Unit PHA9/W

Copyright © 2003 AQA and its licensors. All rights reserved.

The Assessment and Qualifications Alliance (AQA) is a company limited by guarantee registered in England and Wales 3644723 and a registered charity number 1073334
Registered address: Addleshaw Booth & Co., Sovereign House, PO Box 8, Sovereign Street, Leeds LS1 1HQ
Kathleen Tattersall: *Director General*

Unit 9: Electronics

Instructions to examiners

- 1 Give due credit to alternative treatments which are correct. Give marks for what is correct; do not deduct marks because the attempt falls short of some ideal answer. Where marks are to be deducted for particular errors specific instructions are given in the marking scheme.
- 2 Do not deduct marks for poor written communication. Refer the script to the Awards meeting if poor presentation forbids a proper assessment. In each paper candidates may be awarded up to two marks for the Quality of Written Communication in cases of required explanation or description. Use the following criteria to award marks:
 - 2 marks: Candidates write legibly with accurate spelling, grammar and punctuation; the answer containing information that bears some relevance to the question and being organised clearly and coherently. The vocabulary should be appropriate to the topic being examined.
 - 1 mark: Candidates write with reasonably accurate spelling, grammar and punctuation; the answer containing some information that bears some relevance to the question and being reasonably well organised. Some of the vocabulary should be appropriate to the topic being examined.
 - 0 marks: Candidates who fail to reach the threshold for the award of one mark.
- 3 An arithmetical error in an answer should be marked AE thus causing the candidate to lose one mark. The candidate's incorrect value should be carried through all subsequent calculations for the question and, if there are no subsequent errors, the candidate can score all remaining marks (indicated by ticks). These subsequent ticks should be marked CE (consequential error).
- 4 With regard to incorrect use of significant figures, normally two, three or four significant figures will be acceptable. Exceptions to this rule occur if the data in the question is given to, for example, five significant figures as in values of wavelength or frequency in questions dealing with the Doppler effect, or in atomic data. In these cases up to two further significant figures will be acceptable. The maximum penalty for an error in significant figures is **one mark per paper**. When the penalty is imposed, indicate the error in the script by SF and, in addition, write SF opposite the mark for that question on the front cover of the paper to obviate imposing the penalty more than once per paper.
- 5 No penalties should be imposed for incorrect or omitted units at intermediate stages in a calculation or which are contained in brackets in the marking scheme. Penalties for unit errors (incorrect or omitted units) are imposed only at the stage when the final answer to a calculation is considered. The maximum penalty is **one mark per question**.
- 6 All other procedures, including the entering of marks, transferring marks to the front cover and referrals of scripts (other than those mentioned above) will be clarified at the standardising meeting of examiners.

Section A (common to all Option Modules PHA5/W - PHA9/W)

1

- (a) (use of 'isotope' instead of 'nucleus' not accepted)
 there is equal probability of any nucleus decaying,
 it cannot be known which particular nucleus will decay next,
 it cannot be known at what time a particular nucleus will decay,
 the rate of decay is unaffected by the surrounding conditions,
 it is only possible to estimate the proportion of nuclei decaying
 in the next time interval
 any two statements ✓✓ (2)
- (b) continuous curve starting at 5.5×10^5 Bq
 plus correct 1st half-life (2.6 yrs, 2.75×10^5 Bq) ✓
 correct 2nd half-life (5.2 years, 1.4×10^5 Bq) ✓
 (allow C.E. for incorrect 1st half-life) (2)
- (c)(i) (use of $T_{1/2} = \frac{\ln 2}{\lambda}$ gives) $\lambda = \frac{\ln 2}{2.6 \times 3.15 \times 10^7}$ ✓
 $= 8.5 \times 10^{-9} \text{ (s}^{-1}\text{)}$ ✓ ($8.46 \times 10^{-9} \text{ (s}^{-1}\text{)}$)
- (c)(ii) (use of $\frac{dN}{dt} = -\lambda N$ gives) $N = \frac{5.5 \times 10^5}{8.5 \times 10^{-9}}$ ✓
 $= 6.5 \times 10^{13} \text{ (atoms)}$ ✓
 (allow C.E. for value of λ from (i))
- (c)(iii) (use of $N = N_0 e^{-\lambda t}$ and $A \propto N$ gives)
 $t \left(= \frac{\ln(A_0 / A)}{\lambda} \right) = \frac{\ln(1.0 \times 10^5 / 0.75 \times 10^5)}{8.5 \times 10^{-9}}$ ✓
 $= 3.4 \times 10^7 \text{ (s)}$ ✓
 (allow C.E. for value of λ from (i))

(6)
 (10)

Section B

2

(a)(i) $V_o = 10\sqrt{2} = 14.1 \text{ (V)}$ ✓

(a)(ii) peak across resistor = $14.1 - 0.6 = 13.5 \text{ (V)}$ ✓

period = 20 (ms) ✓

diagram of oscilloscope trace to show:

rectified wave ✓

correct peak value ✓

(allow C.E. from calculation above)

correct period ✓

(allow C.E. from calculation above)

max(5)

(b)(i) LED Q lights ✓

Q is in same direction as diode D_2 , (which conducts) ✓

(b)(ii) voltage across R = $13.5 - 2.0 = 11.5 \text{ (V)}$ ✓

$$R = \frac{11.5}{25 \times 10^{-3}} = 460 \text{ (}\Omega\text{)}$$
 ✓

(allow C.E. for R from calculation above)

from E24 series, $R = 470 \Omega$ ✓

(allow C.E. from calculated value of R)

(5)

(10)

3

(a) high input impedance
very large voltage gain
low output impedance

any two ✓✓

(2)

(b)(i) circuit diagram to show: correct feedback and output ✓
correct inputs ✓

(b)(ii) $R_a \geq 1 \text{ k}\Omega$ ✓

gives $R_f = 150 \text{ k}\Omega$ ✓

(4)

(c)(i) fraction of output fed back through R_f ✓
is 180° out of phase with input ✓

(c)(ii) increased stability or less distortion or controlled gain ✓

(c)(iii) range of frequencies within which voltage gain
does not fall by $1/\sqrt{2}$ or power by $1/2$ ✓

(c)(iv) bandwidth given by gain of $\frac{22}{\sqrt{2}} = 16$ ✓ (15.6)

horizontal line at gain = 16 and inside curve ✓

max(5)
(11)

4


(a)(i) time constant of circuit = $200 \times 10^3 \times 0.01 \times 10^{-6} = 2.0 \times 10^{-2} \text{ s}$ ✓

(a)(ii) $RC \ll$ period of the pulse ✓
 when pulse applied $V_R = V_{in}$ ($V_C = 0$) ✓
 C charges quickly ✓
 V_R drops quickly ✓
 when V_{in} returns to zero, capacitor discharges in other
 direction to give negative waveform ✓

max(4)

(b)(i) time constant = 0.2 s ✓

(b)(ii)

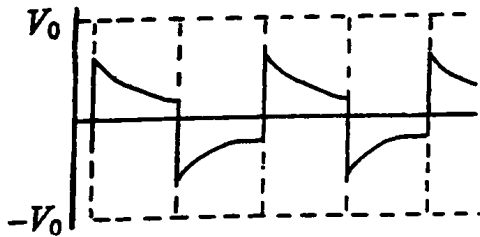

V_{out} less than V_0 ✓
 does not discharge completely ✓
 mirror image negative pulse ✓

(b)(iii) capacitor does not charge or discharge fully ✓

max(3)
 (7)

The Quality of Written Communication marks are to be awarded for the quality
 of answers to Q1(a) and Q2(a) ✓ ✓

(2)
 (2)