



ASSESSMENT and
QUALIFICATIONS
ALLIANCE

Mark scheme

June 2003

GCE

Physics A


Unit PHA9/W

Copyright © 2003 AQA and its licensors. All rights reserved.

Units 5 - 9 : Section A

1

(a)(i)

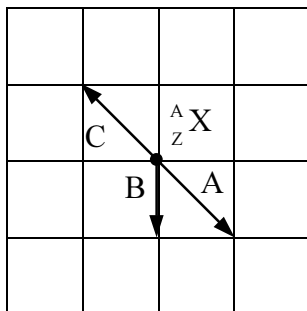

correct arrows: A ✓

B ✓

C ✓

(a)(ii) $e^{-1} + {}^A_ZX \rightarrow {}^A_{Z-1}Y + \nu_e$ ✓ (4)

(b)(i) $((4.18 - 1.33) \times 10^{-13}) = 2.85 \times 10^{-13}$ (J) ✓

(b)(ii) 1.33×10^{-13} (J)
 0.30×10^{-13} (J) for 3 correct values ✓
 1.63×10^{-13} (J)

(b)(iii) (use of $\Delta E = hf$ gives) $f \left(= \frac{1.63 \times 10^{-13}}{6.63 \times 10^{-34}} \right) = 2.46 \times 10^{20}$ Hz ✓

(allow C.E. from (b)(ii) if largest value taken) (3)

(c)(i) (✓ for each precaution with reason to $\text{max}2$)

handle with (long) (30 cm) tweezers
 because the radiation intensity decreases with distance

store in a lead box (immediately) when not in use
 to avoid unnecessary exposure to radiation

[or any sensible precaution with reason]

(b)(ii) γ rays are more penetrating and are therefore more hazardous
 (to the internal organs of the body)

β^- particles are more hazardous because they are more ionising ✓
 (✓ for any argued case for either radiation)

(3)
(10)

Unit 9 : PHA9/W : Section B

2

- (a)(i) suitable scales ✓
 correctly plotted points ✓
 straight line ✓

(a)(ii) (use of $X_C = \frac{1}{2\pi fC}$ gives) $V = \frac{I}{2\pi fC}$ ✓

$$C = \frac{I}{f} \times \frac{1}{2\pi V} = \text{gradient} \times \frac{1}{2\pi V} \quad \checkmark$$

$$[\text{gradient} \left(= \frac{I}{f} \right) = 20\pi C]$$

$$C = \frac{18.2 \times 10^{-3}}{1600} \times \frac{1}{2\pi 10} = 0.18 \mu\text{F} \quad \checkmark \quad \text{max}(5)$$

- (b)(i) at high f , reactance, X_C , has a low value (compared to R) ✓
 most of voltage dropped across R making V_{out} small ✓

(b)(ii) when $X_C = R$, $f = \frac{1}{2\pi RC}$ ✓

$$f = \frac{1}{2\pi 2 \times 10^3 \times 0.18 \times 10^{-6}} = 442 \text{ Hz} \quad \checkmark$$

(allow C.E. for value of C from (a)(ii))

- (b)(iii) for $f \ll 440 \text{ Hz}$, $V_{\text{out}} \approx V_{\text{in}}$ ✓

$$\frac{V_{\text{out}}}{V_{\text{in}}} \rightarrow 1 \quad \checkmark$$

$$\left[\text{or } \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{\sqrt{1 + f^2 / f_0^2}} \right]$$

max(5)

(10)

3

- (a)(i) potential at P is very low $\approx 0.2 \text{ V}$ (or 0 V) ✓

- (a)(ii) TR is off ✓

\therefore no current through relays (alarm off) ✓

(3)

- (b) potential at P goes high (12 V) ✓ [or $> 0.7 \text{ V}$]
 TR conducts ✓

current through relays and alarm switches on ✓

max(2)

(c) TR off
[or transistor by-passed] ✓
still a current through relay ✓ (2)

(d) protects the transistor ✓ (1)
(8)

4

(a) $V_- = 12 \times \frac{30}{46}$ ✓
 $= 7.8 \text{ V}$ ✓ (2)

(b)(i) between V_{out} and 0 V ✓
(or from +12 V to V_{out})
correct direction and resistor ✓

(b)(ii) (since $V_{\text{in}} < \text{switching voltage}$) $V_{\text{out}} = -12 \text{ V}$ (12 V across LED) ✓
(or alternative)

(b)(iii) voltage across R = $(12 - 2) = 10 \text{ (V)}$ ✓
 $10 = 25 \times 10^{-3} \times R$ gives $R = 400 \text{ } \Omega$ ✓ (5)
(or alternatively $22 = 25 \times 10^{-3}$ to give $R = 880 \text{ } \Omega$)

(c) to switch LED voltage at B = 7.8 (V) ✓
 R_{LDR} given by $7.8 = \frac{12 \times 47}{(47 + R)}$ or ✓
 $R_{\text{LDR}} = 25.(3) \text{ k}\Omega$ ✓
light level = 30 lux ✓ max(3)
(10)

QWC marks given for Q1(c)(i) and Q2(b) (2)
(2)