



A-level PHYSICS 7408/3BE

Paper 3 Section B Electronics

Mark scheme

June 2025

Version: 1.0 Final



Mark schemes are prepared by the Lead Assessment Writer and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation events which all associates participate in and is the scheme which was used by them in this examination. The standardisation process ensures that the mark scheme covers the students' responses to questions and that every associate understands and applies it in the same correct way. As preparation for standardisation each associate analyses a number of students' scripts. Alternative answers not already covered by the mark scheme are discussed and legislated for. If, after the standardisation process, associates encounter unusual answers which have not been raised they are required to refer these to the Lead Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of students' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

No student should be disadvantaged on the basis of their gender identity and/or how they refer to the gender identity of others in their exam responses.

A consistent use of 'they/them' as a singular and pronouns beyond 'she/her' or 'he/him' will be credited in exam responses in line with existing mark scheme criteria.

Further copies of this mark scheme are available from aqa.org.uk

Copyright information

AQA retains the copyright on all its publications. However, registered schools/colleges for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to schools/colleges to photocopy any material that is acknowledged to a third party even for internal use within the centre.

Copyright © 2025 AQA and its licensors. All rights reserved.

Physics - Mark scheme instructions to examiners

1. General

The mark scheme for each question shows:

- the marks available for each part of the question
- the total marks available for the question
- the typical answer or answers which are expected
- extra information to help the Examiner make his or her judgement and help to delineate what is acceptable or not worthy of credit or, in discursive answers, to give an overview of the area in which a mark or marks may be awarded.

The extra information is aligned to the appropriate answer in the left-hand part of the mark scheme and should only be applied to that item in the mark scheme.

At the beginning of a part of a question a reminder may be given, for example: where consequential marking needs to be considered in a calculation; or the answer may be on the diagram or at a different place on the script.

In general the right-hand side of the mark scheme is there to provide those extra details which confuse the main part of the mark scheme yet may be helpful in ensuring that marking is straightforward and consistent.

2. Emboldening

2.1

In a list of acceptable answers where more than one mark is available ‘any **two** from’ is used, with the number of marks emboldened. Each of the following bullet points is a potential mark.

2.2

A bold **and** is used to indicate that both parts of the answer are required to award the mark.

2.3

Alternative answers acceptable for a mark are indicated by the use of **or**. Different terms in the mark scheme are shown by a / ; eg allow smooth / free movement.

3. Marking points

3.1 Marking of lists

This applies to questions requiring a set number of responses, but for which candidates have provided extra responses. The general principle to be followed in such a situation is that ‘right + wrong = wrong’.

Each error/contradiction negates each correct response. So, if the number of errors/contradictions equals or exceeds the number of marks available for the question, no marks can be awarded.

However, responses considered to be neutral (often prefaced by ‘Ignore’ in the mark scheme) are not penalised.

3.2 Marking procedure for calculations

Full marks can usually be given for a correct numerical answer without working shown unless the question states 'Show your working'. However, if a correct numerical answer can be evaluated from incorrect physics then working will be required. The mark scheme will indicate both this and the credit (if any) that can be allowed for the incorrect approach.

However, if the answer is incorrect, mark(s) can usually be gained by correct substitution/working and this is shown in the 'extra information' column or by each stage of a longer calculation.

A calculation must be followed through to answer in decimal form. An answer in surd form is never acceptable for the final (evaluation) mark in a calculation and will therefore generally be denied one mark.

3.3 Interpretation of 'it'

Answers using the word 'it' should be given credit only if it is clear that the 'it' refers to the correct subject.

3.4 Errors carried forward, consequential marking and arithmetic errors

Allowances for errors carried forward are likely to be restricted to calculation questions and should be shown by the abbreviation ECF or *conseq* in the marking scheme.

An arithmetic error should be penalised for one mark only unless otherwise amplified in the marking scheme. Arithmetic errors may arise from a slip in a calculation or from an incorrect transfer of a numerical value from data given in a question.

3.5 Phonetic spelling

The phonetic spelling of correct scientific terminology should be credited (eg fizix) **unless** there is a possible confusion (eg defraction/refraction) with another technical term.

3.6 Brackets

(.....) are used to indicate information which is not essential for the mark to be awarded but is included to help the examiner identify the sense of the answer required.

3.7 Ignore / Insufficient / Do not allow

'Ignore' or 'insufficient' is used when the information given is irrelevant to the question or not enough to gain the marking point. Any further correct amplification could gain the marking point.

'Do **not** allow' means that this is a wrong answer which, even if the correct answer is given, will still mean that the mark is not awarded.

3.8 Significant figure penalties

Answers to questions in the practical sections (7407/2 – Section A and 7408/3A) should display an appropriate number of significant figures. For non-practical sections, an A-level paper may contain up to 2 marks (1 mark for AS) that are contingent on the candidate quoting the **final** answer in a calculation to a specified number of significant figures (sf). This will generally be assessed to be the number of sf of the datum with the least number of sf from which the answer is determined. The mark scheme will give the range of sf that are acceptable but this will normally be the sf of the datum (or this sf –1).

An answer in surd form cannot gain the sf mark. An incorrect calculation **following some working** can gain the sf mark. For a question beginning with the command word 'Show that...', the answer should be quoted to **one more** sf than the sf quoted in the question eg 'Show that X is equal to about 2.1 cm' – answer should be quoted to 3 sf. An answer to 1 sf will not normally be acceptable, unless the answer is an integer eg a number of objects. In non-practical sections, the need for a consideration will be indicated in the question by the use of 'Give your answer to an appropriate number of significant figures'.

3.9 Unit penalties

An A-level paper may contain up to 2 marks (1 mark for AS) that are contingent on the candidate quoting the correct unit for the answer to a calculation. The need for a unit to be quoted will be indicated in the question by the use of 'State an appropriate SI unit for your answer'. Unit answers will be expected to appear in the most commonly agreed form for the calculation concerned; strings of fundamental (base) units would not. For example, 1 tesla and 1 Wb m⁻² would both be acceptable units for magnetic flux density but 1 kg m² s⁻² A⁻¹ would not.

3.10 Level of response marking instructions

Level of response mark schemes are broken down into three levels, each of which has a descriptor. The descriptor for the level shows the average performance for the level. There are two marks in each level.

Before you apply the mark scheme to a student's answer read through the answer and annotate it (as instructed) to show the qualities that are being looked for. You can then apply the mark scheme.

Determining a level

Start at the lowest level of the mark scheme and use it as a ladder to see whether the answer meets the descriptor for that level. The descriptor for the level indicates the different qualities that might be seen in the student's answer for that level. If it meets the lowest level then go to the next one and decide if it meets this level, and so on, until you have a match between the level descriptor and the answer. With practice and familiarity you will find that for better answers you will be able to quickly skip through the lower levels of the mark scheme.

When assigning a level you should look at the overall quality of the answer and not look to pick holes in small and specific parts of the answer where the student has not performed quite as well as the rest. If the answer covers different aspects of different levels of the mark scheme you should use a best fit approach for defining the level and then use the variability of the response to help decide the mark within the level, ie if the response is predominantly level 2 with a small amount of level 3 material it would be placed in level 2.

The exemplar materials used during standardisation will help you to determine the appropriate level. There will be an answer in the standardising materials which will correspond with each level of the mark scheme. This answer will have been awarded a mark by the Lead Examiner. You can compare the student's answer with the example to determine if it is the same standard, better or worse than the example. You can then use this to allocate a mark for the answer based on the Lead Examiner's mark on the example.

You may well need to read back through the answer as you apply the mark scheme to clarify points and assure yourself that the level and the mark are appropriate.

Indicative content in the mark scheme is provided as a guide for examiners. It is not intended to be exhaustive and you must credit other valid points. Students do not have to cover all of the points mentioned in the indicative content to reach the highest level of the mark scheme.

An answer which contains nothing of relevance to the question must be awarded no marks.

Question	Answers	Additional comments/Guidance	Mark	AO
01.1	The diagram shows two 4-bit binary counters. The first counter's clock (CK) is connected to a 1 Hz signal. Its reset (R) input is connected to an OR gate with inputs from Q1 and Q3. The output of the first counter's Q3 is connected to the clock (CK) of the second counter. The second counter's reset (R) input is connected to an OR gate with inputs from Q1 and Q2. A manual reset switch (S) is connected to the reset inputs of both counters through a resistor. The circuit is powered by 9V and 0V rails.	Condone lack of connection blobs. 1 mark for correct reset codes for each counter ✓ (Q₁ and Q₃ for LH counter, Q₁ and Q₂ for RH counter) 1 mark for AND gates used with reset codes ✓ 1 mark for correct link between counters ✓ 1 mark for correct resistor - switch arrangement used for manual reset ✓ 1 mark for OR gates used to provide all reset conditions for each counter ✓	5	2 × AO2 3 × AO3

Question	Answers	Additional comments/Guidance	Mark	AO
01.2		Condone no connection blobs on this occasion. mp1 for (X AND Y) OR ✓ mp2 for Z AND ((NOT X) NAND (NOT Y)) ✓ No penalty after final AND gate in mp2	2	AO2

Question	Answers	Additional comments/Guidance	Mark	AO
01.3	AND ✓		1	AO2
Total			8	

Question	Answers	Additional comments/Guidance	Mark	AO
02.1	Accept either: ✓ • determines the charging / discharging rate of the capacitor • determines the oscillation frequency	Condone reference to charging/discharging of the capacitor.	1	AO1


Question	Answers	Additional comments/Guidance	Mark	AO
02.2	(The three 100 kΩ resistors together) set the reference voltage(s) (at the non-inverting terminal) ✓		1	AO2

Question	Answers	Additional comments/Guidance	Mark	AO
02.3	Evidence of a parallel resistor calculation or a potential divider calculation ✓ when V_{out} is 0.0 V, $V_+ = 3.0 \text{ V}$ ✓ when V_{out} is 9.0 V, $V_+ = 6.0 \text{ V}$ ✓		3	2 × AO2 1 × AO3

Question	Answers	Additional comments/Guidance	Mark	AO
02.4	PRF = 62.5 kHz ✓ (accept 63 kHz) Duty cycle = 37.5% ✓ (accept 38%)	$\left(PRF = \frac{1}{t_H + t_L} = \frac{1.0 \times 10^6}{(6 + 10)} \right)$ $duty\ cycle = \frac{t_H}{t_H + t_L} \times 100\%$ $= \frac{6}{6 + 10} \times 100\%$	2	AO3
Total			7	

Question	Answers	Additional comments/Guidance	Mark	AO
03.1	One from: ✓ • shorter response time • current varies linearly with illumination	Accept other correct answers.	1	AO1

Question	Answers	Additional comments/Guidance	Mark	AO
03.2	A virtual earth is a point that sits at 0 V (due to the configuration of the circuit) even though there is no direct physical connection to ground ✓ OWTTE	Accept the idea that it acts as if grounded.	1	AO1

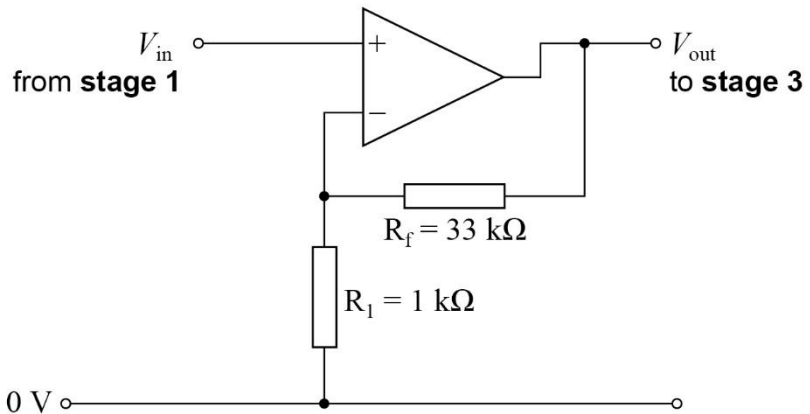Question	Answers	Additional comments/Guidance	Mark	AO
03.3		Condone lack of connection blobs on this occasion. Condone the use of an input resistor on the non-inverting input but cannot be used as part of gain calculation. mp1 - general configuration for operational amplifier giving a non-inverting amplification including correctly labelled input terminals ✓ mp2 - use of resistors within the defined range giving $\frac{R_f}{R_1} = +33$ ✓	2	AO2

Question	Answers	Additional comments/Guidance	Mark	AO
03.4	Identify that the switching voltage in stage 3 is 6.8 V. Output from stage 1 must be $\frac{6.8}{34} = 0.2 \text{ V}$ ✓₁ I_D in stage 1 is $\frac{\text{their MP1 value}}{10 \text{ k}\Omega}$ ✓₂ Uses their mp2 value to calculate an irradiance from the graph. ✓₃	Expect to see $I_D (= 20 \mu\text{A})$ ✓₂ Expect to see an irradiance of (4 W m^{-2}) ✓₃	3	AO3

Question	Answers	Additional comments/Guidance	Mark	AO
03.5	The idea that real op amps may saturate at a value $> 0 \text{ V}$ (This may leave sufficient voltage to activate the LED) ✓		1	AO2
Total			8	

Question	Answers	Additional comments/Guidance	Mark	AO
04.1	A carrier wave is a fixed frequency (radio wave assigned to a radio station and used to transmit information/signal) ✓ Some aspect of the carrier wave characteristic (eg amplitude / frequency) must be varied / modulated (to represent the information / signal being transmitted) OWTTE ✓		2	AO1

Question	Answers	Additional comments/Guidance	Mark	AO
04.2	The circuit will resonate at a particular frequency (based upon the values of L and C) ✓₁ The idea that the circuit acts as a filter. (The signal with this frequency will have a large amplitude across the LC circuit compared with other signals received by the aerial. OWTTE OR Varying (L or) C will change the resonant frequency of the circuit and hence the station selected (from those received by the aerial) ✓₂	If filter is not mentioned, accept explanation.	2	AO1

Question	Answers	Additional comments/Guidance	Mark	AO
04.3	Both circuits can accommodate the required bandwidth. (Some evidence that this has been calculated for at least one circuit) ✓₁ Circuit A chosen Consistent explanation ✓₂ .	May be inferred from the calculations and values Expect to see: Bandwidth A = 12 kHz ± 2 kHz Bandwidth B = 24 kHz ± 2 kHz Expect to see: Sharper peak indicates high Q factor hence less interference from other stations Do not accept reference to Q factor alone	2	AO3
Total			6	

Question	Answers	Additional comments/Guidance	Mark	AO						
05	The mark scheme gives some guidance as to what statements are expected to be seen in a 1- or 2-mark (L1), 3- or 4-mark (L2) and 5- or 6-mark (L3) answer. Guidance provided in section 3.10 of the <i>Mark Scheme Instructions</i> document should be used to assist in marking this question. <table><tr><th>Mark</th><th>Criteria</th></tr><tr><td>6</td><td>All three pathways covered in some detail. 6 marks can be awarded even if there is an error and /or parts of one aspect missing.</td></tr><tr><td>5</td><td>All three pathways covered, at least two in detail. Whilst there will be gaps, there should only be an occasional error.</td></tr></table>	Mark	Criteria	6	All three pathways covered in some detail. 6 marks can be awarded even if there is an error and /or parts of one aspect missing.	5	All three pathways covered, at least two in detail. Whilst there will be gaps, there should only be an occasional error.	Ground waves (surface waves) • use long waves (LW) 150 kHz to 300 kHz (wavelength 1 km to 2 km) • waves are diffracted by Earth’s surface – travel along curvature. Advantages • large area of coverage for given power • absorption of E-M wave is less at low frequency Disadvantages • may still be receivers in geographical shadows • attenuation with distance • LW - only able to carry limited information due to restricted bandwidth Accept medium wave (MW) 300 kHz to 3 MHz (0.1 to 1 km) Disadvantage • attenuation in this band increases with increase in frequency • diffraction may be less prominent hence more shadows in the higher end of this band	6	AO1
Mark	Criteria									
6	All three pathways covered in some detail. 6 marks can be awarded even if there is an error and /or parts of one aspect missing.									
5	All three pathways covered, at least two in detail. Whilst there will be gaps, there should only be an occasional error.									

	Mark	Criteria	Sky waves • use short wave (SW) 3 MHz to 30 MHz (wavelength 10 m to 100 m) • for $f > 0.5$ MHz, ionosphere reflects radio waves • radio wave is refracted by ionosphere sufficiently to be returned as if reflected Advantages • wavelength too short to suffer diffraction • attenuation is low due to the use of high frequencies Disadvantages • ionosphere susceptible to Sun activity • signal reception fade due to unstable ionosphere Space waves • use microwaves 2 GHz to 100 GHz (wavelength 3 mm to 150 mm) • microwave connects with satellite (uplink) using line of sight • signal transmitted down to Earth station using different frequency (down link) Advantages • wavelength too short to suffer diffraction • short wavelength penetrates atmosphere and the ionosphere • large bandwidth available • satellite able to transmit to multiple receivers over large geographical area Disadvantages • damp atmosphere can cause microwave attenuation • initial capital cost is higher than for other pathways		
	4	Two areas successfully discussed, or one discussed and two others covered partially. Whilst there will be several gaps, there should only be an occasional error.			
	3	One area discussed and one discussed partially, or all three covered partially. There are likely to be several errors and omissions in the discussion.			
	2	Only one pathway discussed or makes a partial attempt at two pathways.			
	1	None of the three pathways covered without significant error.			
	0	The answer contains no creditable analysis of the question.			
Total				6	